

# Sheet 8

Digdarshan Kunwar

November 15, 2018

## Problem 8

A full adder digital circuit was introduced in class. It is defined by the following two Boolean functions:

$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = (A \wedge B) \vee (C_{in} \wedge (A \oplus B))$$

Making the truth table :

A	B	$C_{in}$	S	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

a) Write both functions as a (short) disjunction of product terms.

Here,

We know that,

$$A \oplus B = \neg(A \wedge B) \wedge (A \vee B)$$
$$= (\neg A \vee \neg B) \wedge (A \vee B)$$
$$= (A \wedge \neg B) \vee (\neg A \wedge B)$$

$$S = A \oplus B \oplus C_{in}$$

We can also write it as :

$$S = A \oplus B \oplus C_{in}$$
$$= ((A \wedge \neg B) \vee (\neg A \wedge B)) \oplus C_{in}$$
$$= (\neg((A \wedge \neg B) \vee (\neg A \wedge B)) \wedge C_{in}) \vee (((A \wedge \neg B) \vee (\neg A \wedge B)) \wedge \neg C_{in})$$
$$= ((\neg(A \wedge \neg B) \wedge \neg(\neg A \wedge B)) \wedge C_{in}) \vee (((A \wedge \neg B) \vee (\neg A \wedge B)) \wedge \neg C_{in})$$
$$= (((\neg A \vee B) \wedge (A \vee \neg B)) \wedge C_{in}) \vee (((A \wedge \neg B) \vee (\neg A \wedge B)) \wedge \neg C_{in})$$
$$= (((\neg A \wedge (A \vee \neg B)) \vee (B \wedge (A \vee \neg B))) \wedge C_{in}) \vee (((A \wedge \neg B) \vee (\neg A \wedge B)) \wedge \neg C_{in})$$
$$= (((\neg A \wedge \neg B) \vee (B \wedge A)) \wedge C_{in}) \vee (((A \wedge \neg B) \vee (\neg A \wedge B)) \wedge \neg C_{in})$$
$$= (\neg A \wedge \neg B \wedge C_{in}) \vee (A \wedge B \wedge C_{in}) \vee (A \wedge \neg B \wedge \neg C_{in}) \vee (\neg A \wedge B \wedge \neg C_{in})$$

For the Second term :

$$\begin{aligned}
C_{out} &= (A \wedge B) \vee (C_{in} \wedge (A \oplus B)) \\
&= (A \wedge B) \vee (C_{in} \wedge ((A \wedge \neg B) \vee (\neg A \wedge B))) \\
&= (A \wedge B) \vee ((C_{in} \wedge (A \wedge \neg B)) \vee (C_{in} \wedge (\neg A \wedge B))) \\
&= (A \wedge B) \vee ((C_{in} \wedge A \wedge \neg B) \vee (C_{in} \wedge \neg A \wedge B)) \\
&= (A \wedge B) \vee ((C_{in} \wedge A \wedge \neg B) \vee (C_{in} \wedge \neg A \wedge B)) \\
&= (A \vee ((C_{in} \wedge A \wedge \neg B) \vee (C_{in} \wedge \neg A \wedge B))) \wedge (B \vee ((C_{in} \wedge A \wedge \neg B) \vee (C_{in} \wedge \neg A \wedge B))) \\
&= (A \vee (C_{in} \wedge A \wedge \neg B) \vee A \vee (C_{in} \wedge \neg A \wedge B)) \wedge (B \vee (C_{in} \wedge A \wedge \neg B) \vee B \vee (C_{in} \wedge \neg A \wedge B)) \\
&= (A \vee A \vee (C_{in} \wedge \neg A \wedge B)) \wedge (B \vee B \vee (C_{in} \wedge A \wedge \neg B)) \\
&= (A \vee (C_{in} \wedge \neg A \wedge B)) \wedge (B \vee (C_{in} \wedge A \wedge \neg B)) \\
&= ((A \vee C_{in}) \wedge (A \vee \neg A) \wedge (A \vee B)) \wedge ((B \vee C_{in}) \wedge (B \vee A) \wedge (B \vee \neg B)) \\
&= (A \vee C_{in}) \wedge (A \vee B) \wedge (B \vee C_{in}) \wedge (B \vee A) \\
&= (A \vee C_{in}) \wedge (A \vee B) \wedge (B \vee C_{in}) \\
&= (A \wedge B) \vee (C_{in} \wedge A) \vee (C_{in} \wedge B)
\end{aligned}$$

b) Write both functions as a (short) conjunction of sum terms

Now writing the Boolean functions in CNF Form :

We can reverse the DNF boolean operators ( $\wedge$  to  $\vee$ ) and ( $\vee$  to  $\wedge$ ) to get CNF :

Or we can construct CNF looking at the table. Either way we get the following result.

$$\begin{aligned}
S &= A \oplus B \oplus C_{in} \\
&= (\neg A \vee \neg B \vee C_{in}) \wedge (A \vee B \vee C_{in}) \wedge (A \vee \neg B \vee \neg C_{in}) \wedge (\neg A \vee B \vee \neg C_{in})
\end{aligned}$$

$$\begin{aligned}
C_{out} &= (A \wedge B) \vee (C_{in} \wedge (A \oplus B)) \\
&= (A \wedge B) \vee (C_{in} \wedge ((A \wedge \neg B) \vee (\neg A \wedge B))) \\
&= (A \wedge B) \vee ((C_{in} \wedge (A \wedge \neg B)) \vee (C_{in} \wedge (\neg A \wedge B))) \\
&= (A \wedge B) \vee ((C_{in} \wedge A \wedge \neg B) \vee (C_{in} \wedge \neg A \wedge B)) \\
&= (A \wedge B) \vee ((C_{in} \wedge A \wedge \neg B) \vee (C_{in} \wedge \neg A \wedge B)) \\
&= (A \vee ((C_{in} \wedge A \wedge \neg B) \vee (C_{in} \wedge \neg A \wedge B))) \wedge (B \vee ((C_{in} \wedge A \wedge \neg B) \vee (C_{in} \wedge \neg A \wedge B))) \\
&= (A \vee (C_{in} \wedge A \wedge \neg B) \vee A \vee (C_{in} \wedge \neg A \wedge B)) \wedge (B \vee (C_{in} \wedge A \wedge \neg B) \vee B \vee (C_{in} \wedge \neg A \wedge B)) \\
&= (A \vee A \vee (C_{in} \wedge \neg A \wedge B)) \wedge (B \vee B \vee (C_{in} \wedge A \wedge \neg B)) \\
&= (A \vee (C_{in} \wedge \neg A \wedge B)) \wedge (B \vee (C_{in} \wedge A \wedge \neg B)) \\
&= ((A \vee C_{in}) \wedge (A \vee \neg A) \wedge (A \vee B)) \wedge ((B \vee C_{in}) \wedge (B \vee A) \wedge (B \vee \neg B)) \\
&= (A \vee C_{in}) \wedge (A \vee B) \wedge (B \vee C_{in}) \wedge (B \vee A) \\
&= (A \vee C_{in}) \wedge (A \vee B) \wedge (B \vee C_{in})
\end{aligned}$$

c) Write both functions using only not ( $\neg$ ) and not-and ( $\uparrow$ ) operations.

We take the DNF of ther functions :

So, now

For term  $S = A \oplus B \oplus C_{in}$

$$\begin{aligned}
S &= A \oplus B \oplus C_{in} \\
&= (\neg A \wedge \neg B \wedge C_{in}) \vee (A \wedge B \wedge C_{in}) \vee (A \wedge \neg B \wedge \neg C_{in}) \vee (\neg A \wedge B \wedge \neg C_{in}) \\
&= \neg \neg ((\neg A \wedge \neg B \wedge C_{in}) \vee (A \wedge B \wedge C_{in}) \vee (A \wedge \neg B \wedge \neg C_{in}) \vee (\neg A \wedge B \wedge \neg C_{in})) \\
&= \neg (\neg (\neg A \wedge \neg B \wedge C_{in}) \wedge \neg (A \wedge B \wedge C_{in}) \wedge \neg (A \wedge \neg B \wedge \neg C_{in}) \wedge \neg (\neg A \wedge B \wedge \neg C_{in})) \\
&= (\neg (\neg A \wedge \neg B \wedge C_{in}) \uparrow \neg (A \wedge B \wedge C_{in}) \uparrow \neg (A \wedge \neg B \wedge \neg C_{in}) \uparrow \neg (\neg A \wedge B \wedge \neg C_{in})) \\
&= (\neg A \uparrow \neg B \uparrow C_{in}) \uparrow (A \uparrow B \uparrow C_{in}) \uparrow (A \uparrow \neg B \uparrow \neg C_{in}) \uparrow (\neg A \uparrow B \uparrow \neg C_{in})
\end{aligned}$$

For the Second term:

$$\begin{aligned}
C_{out} &= (A \wedge B) \vee (C_{in} \wedge (A \oplus B)) \\
&= (A \wedge B) \vee (C_{in} \wedge A) \vee (C_{in} \wedge B) \\
&= \neg \neg ((A \wedge B) \vee (C_{in} \wedge A) \vee (C_{in} \wedge B)) \\
&= \neg (\neg (A \wedge B) \wedge \neg (C_{in} \wedge A) \wedge \neg (C_{in} \wedge B)) \\
&= \neg ((A \uparrow B) \wedge (C_{in} \uparrow A) \wedge (C_{in} \uparrow B)) \\
&= ((A \uparrow B) \uparrow (C_{in} \uparrow A) \uparrow (C_{in} \uparrow B)) \\
&= (A \uparrow B) \uparrow (C_{in} \uparrow A) \uparrow (C_{in} \uparrow B)
\end{aligned}$$

d) In a digital circuit, we can easily reuse common terms. Draw a small digital circuit implementing S and  $C_{out}$  using NAND gates only.

•  $S = A \oplus B \oplus C_{in}$

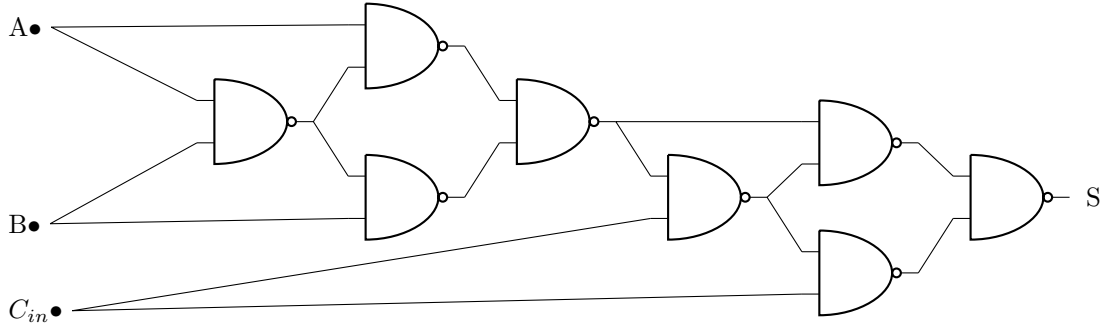


Fig 1

•  $C_{out} = (A \wedge B) \vee (C_{in} \wedge (A \oplus B))$

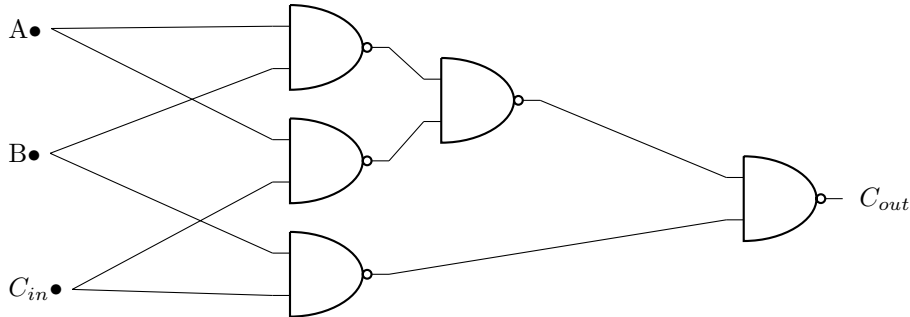


Fig 2

Note : Here in the Fig 2 any input originating from A B C do not intersect with the inputs originating from any other different inputs.(ie:there is no intersection of two different inputs).